

Simple-As-Possible (SAP-1) part 1

SAP1 Malvino.pdf


SAP-1

- The Simple-As-Possible (SAP)-1 computer is a very basic model of a microprocessor explained.
- The SAP-1 design contains the basic necessities for a functional Microprocessor.
- Its primary purpose is to develop a basic understanding of how a microprocessor works, interacts with memory and other parts of the system like input and output.
- The instruction set is very limited and is simple.
- SAP is Simple-As-Possible Computer. The type of computer is specially designed for the academic purpose and nothing has to do with the commercial use.

SAP-1

 - The architecture is **8 bits** and comprises of **16 X 8 memory**. 16 memory location with 8 bits in each location. All instructions (**5 only**) get stored in this memory. It means SAP cannot store program having more than 16 instructions.
- SAP can only perform addition and subtraction and no logical operation. These arithmetic operations are performed by an adder/subtractor unit.






- SAP1*
- main
- Control Sequencer
- C39
- C40
- C41
- C43
- Decoder
- Base
- Poke Tool
- Edit Tool
- Select Tool
- Wiring Tool
- Text Tool
- Menu Tool
- Splitter
- Pin
- Probe
- Clock
- Label
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Button
- Joystick
- Keyboard
- LED
- 7-Segment Display

Facing	South
High Duration	1 Tick
Low Duration	1 Tick
Label	
Label Location	West
Label Font	SansSerif Plain 12

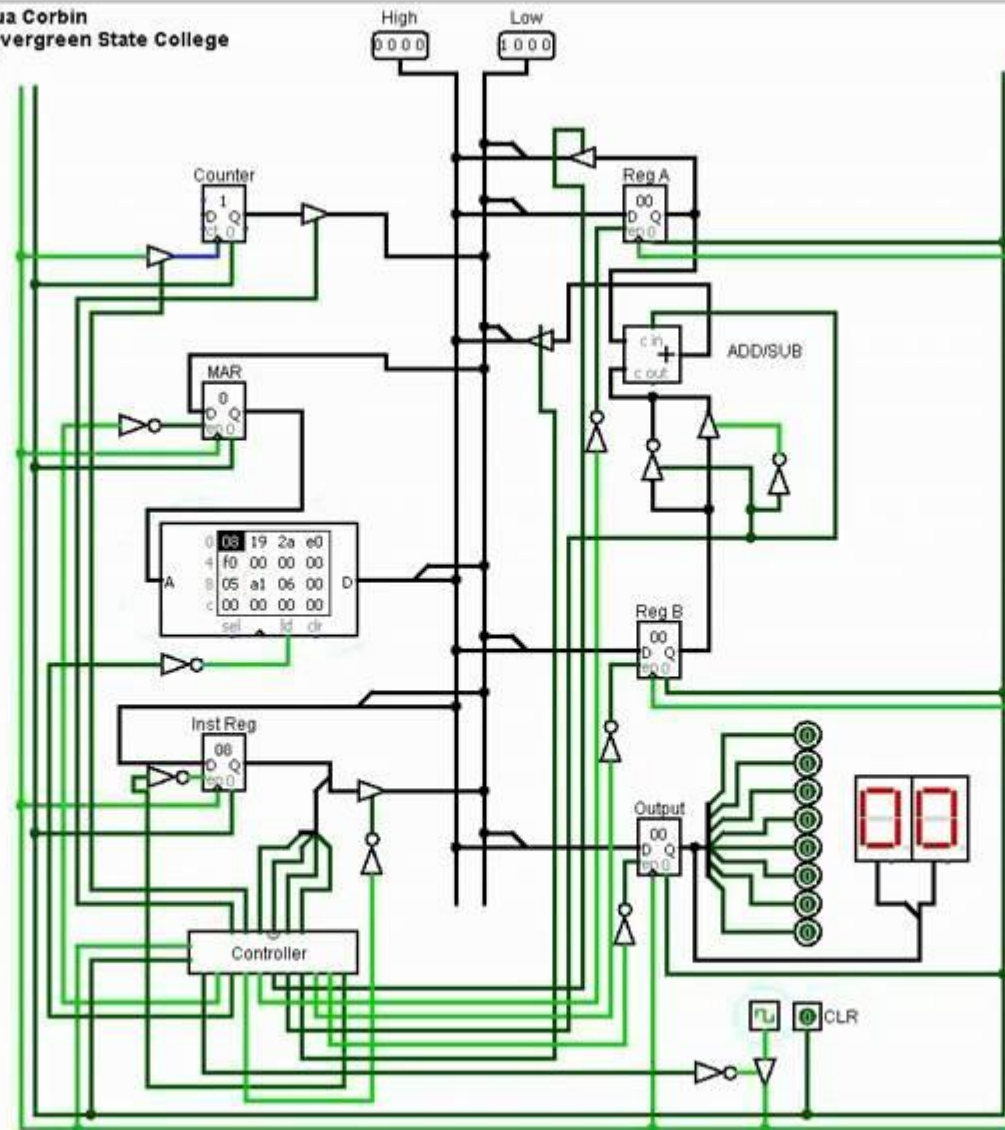Joshua Corbin
The Evergreen State College
SAP-1



Assembly Language Commands


Mnemonic	Binary Op Code
Load A	0000
ADD A	0001
A-B	0010
Output	1110
Halt	1111

Program Currently in Ram

5 + 11 - 6

Mnemonic Commands

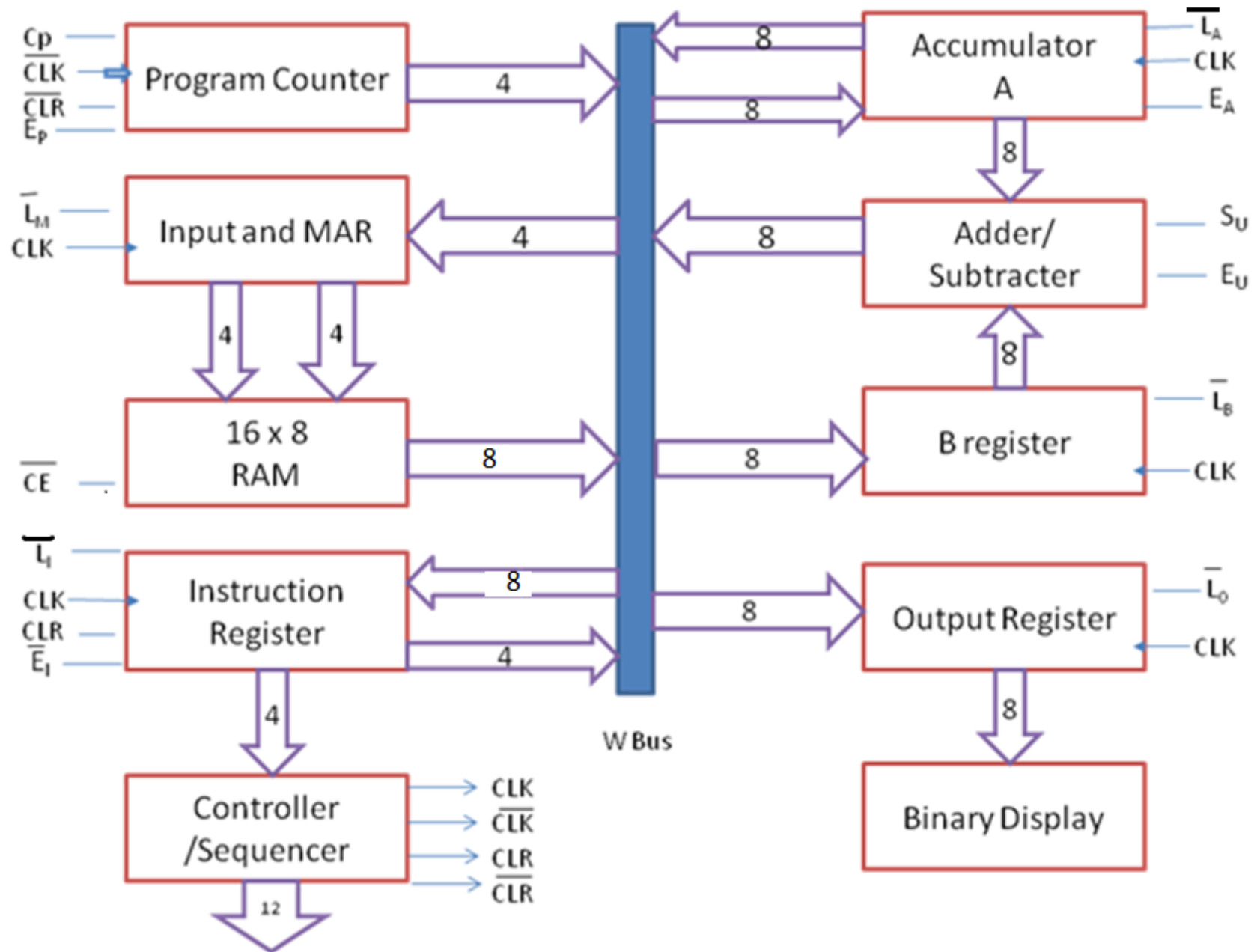Load A from Memory Location 8 (value 05)
Add Memory Location 9 (value 11) to value in Register A (value 05)
Subtract Memory Location 10 (value 6) from Register A (value 16)
Output Value in Register A to LEDs/HEX Display
Halt Program



Block diagram of Simple-As-Possible (SAP)-1 Architecture

$$CON = C_p E_p L'_M CE' \quad L'_I E'_I L'_A E_A \quad S_U E_U L'_B L'_O$$

SAP-1 Architecture

1. Counter Program (Program Counter)
2. Register Input & Memory Address Register (MAR)
3. 16 x 8 RAM memory
4. Register Instructions
5. Control Sequencer (Control Sequencer)
6. Accumulator A
7. Adder / Subtractor
8. Register B
9. Output Register
10. Binary display

SAP-1 Architecture : 1. Program Counter



Function

It's job is to send to the memory the address of the next instruction to be executed and fetched.

- Control Line on Program Counter (PC):
 - Ep : Transfer value from PC to Bus W
 - Cp : Controls increment PC: $PC \leftarrow PC + 1$

SAP-1 Architecture : 1. Program Counter

Process

- 1) The PC is reset to 0000 before each computer run
- 2) When the computer run begins, the PC sends address 0000 to the MAR.
- 3) The pc is then incremented to get 0001.


MAR ← PC

PC ← PC + 1

 - 4) After the first instruction is fetched and executed, the PC sends address 0001 to the memory.

In this way, the PC is keeping track of the next instruction to be executed.

SAP-1 Architecture : 2. Input and MAR (Memory Address Register)




Function

Its job is to hold (latched) the address of PC into Memory Address Register (MAR)

- Control Line on Input and MAR:
 - $\overline{\text{Lm}}$: Retrieving data from bus W into MAR.


SAP-1 Architecture : 2. Input and MAR (Memory Address Register)

MAR \leftarrow [PC]

 

201	LOAD 206
202	ADD #205
203	STORE 205

SAP-1 Architecture : 3. RAM

 

Function

The program code to be executed and data for SAP-1 computer is stored here.

❑ Control Line on RAM:


- $\overline{\text{CE}}$: Removing data 8 bit from memory to bus W.

SAP-1 Architecture : 3. RAM

- Process

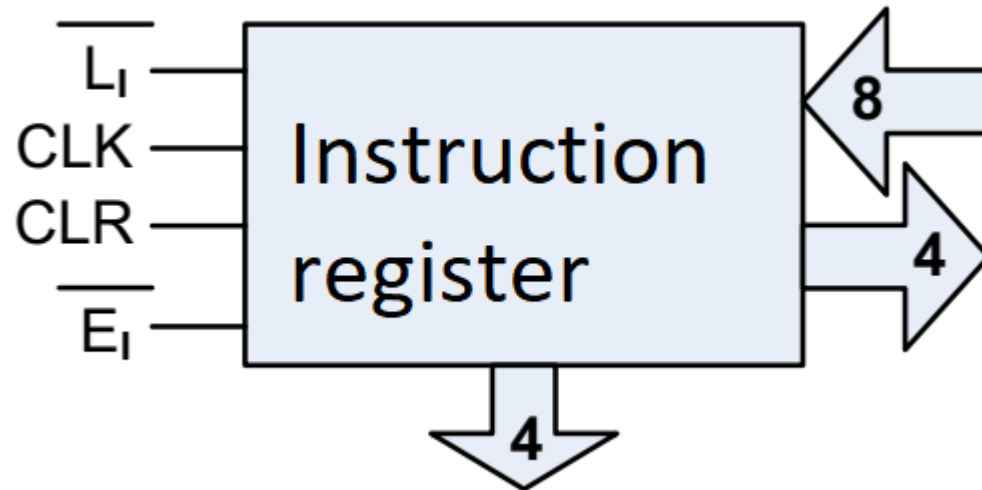- 1) MAR applies 4-bit address to the RAM, where a real read operation is performed
- 2) Thus, the **instruction** or **data** word stored in RAM is placed on the W bus for use by some other part of the computer.

SAP-1 Architecture : 4. Instruction register



Function

IR contains the instruction (composed of OP CODE+ADDRESS) to be executed by SAP1 computer.

□ Control Line on Instruction register:


- \overline{L}_I : Retrieve 8 bit data from bus W.
- \overline{E}_I : Controls 4 bit data from IR to bus W.

SAP-1 Architecture : 4. Instruction register

- Process

 - 1) The contents of the IR are split into two nibbles.
- 2) The upper nibble is a two state output that goes directly to the block labelled 'Controller-sequencer'.
- 3) The lower nibble is send to the W-bus.

SAP-1 Architecture : 5. Controller/Sequences




Function

$C_p E_p \overline{L_M} \overline{C_E} \quad \overline{L_I} \overline{E_I} \overline{L_A} E_A \quad S_U E_U \overline{L_B} \overline{L_O}$

- It generates the control signals for each block so that actions occur in desired sequence. CLK signal is used to synchronize the overall operation of the SAP1 computer.
- A 12-bit word comes out of the Controller-Sequencer block. This control word determines how the registers will react to the next positive CLK edge.

SAP-1 Architecture : 6. Accumulator A

 


Function

- It is a 8-bit buffer register that stores intermediate results during a computer run.
- It is always one of the operands of ADD, SUB and OUT instructions.

☐ Control Line on Accumulator A:

- \overline{L}_A : Retrieve 8 bit data from bus W.
- E_A : Control the 8 bit data into bus W (The value appeared in the W bus)

 
SAP-1 Architecture : 7. Adder / Subtractor



Function

- It is a 2's complement adder-subtractor.
- ❑ Control Line on Adder / Subtractor:
 - S_u : **Low signal (0)** then addition operation, when **signal high (1)** then the operation subtraction.
 - E_u : Send data to bus W


SAP-1 Architecture : 8. Register B

 

Function

- It is 8-bit buffer register which is primarily used to hold the other operand (one operand is always accumulator) of mathematical operations.
- ☐ Control Line on Register B:
- L_b : Retrieve data from bus W to register B


SAP-1 Architecture : 9. Output Register

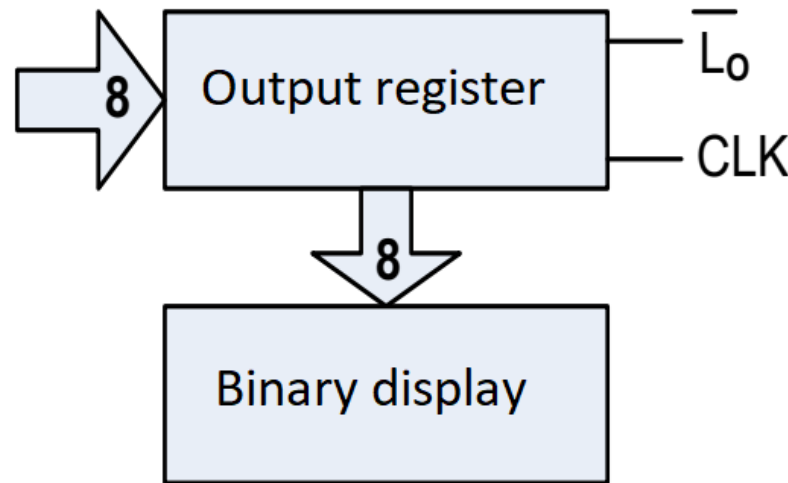

Function

- This registers hold the output of OUT instruction.
- ☐ Control Line on Output Register:
- Lo: Retrieve data 8 bits from bus W

SAP-1 Architecture : 10. Binary display

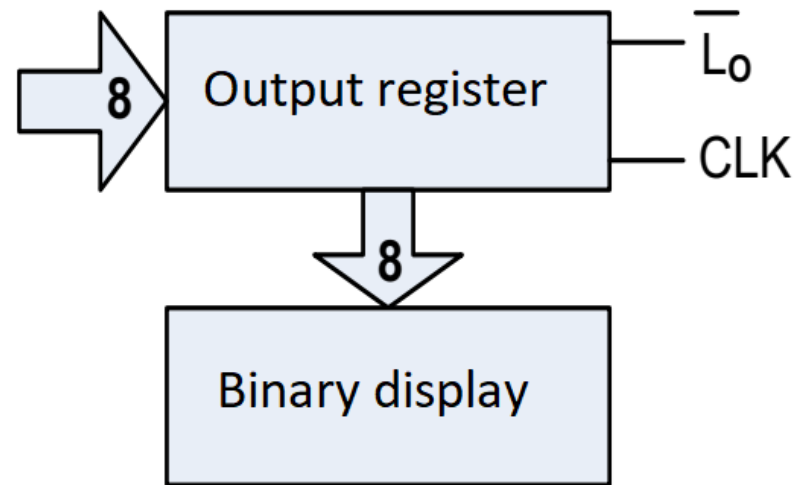

Function

- It is a row of eight LEDs to show the contents of output register.
- Binary display unit is the output device for the SAP-1 microprocessor.

SAP-1 Architecture : Exercise

